

Topic 3: Building the ALU

Processor units

- **ALU** (arithmetic logic unit) : performs arithmetic operations

Registers : to hold data that is being processed


Control unit: fetches each instruction

-



ALU units

Arithmetic and logic operations units:

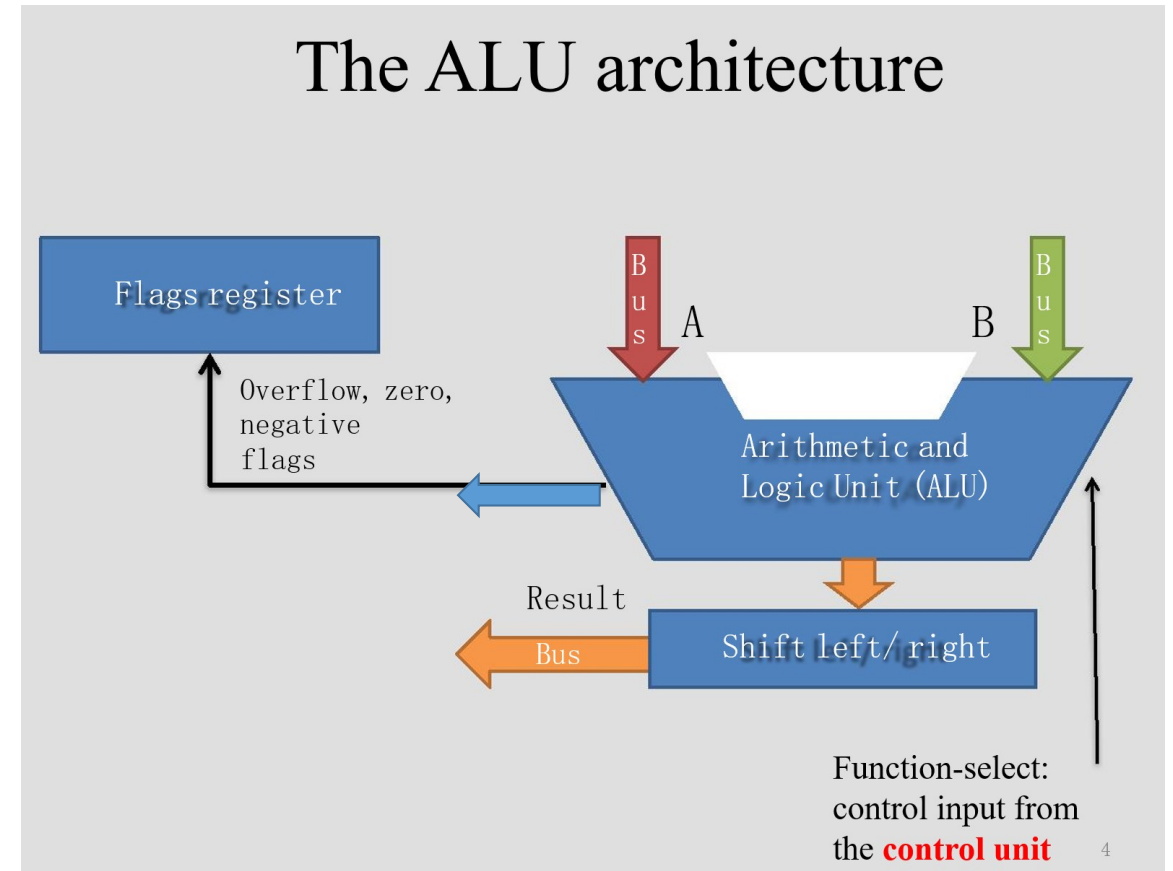- add, subtract, multiply, divide, shift of integers, ...
and, or, not, xor, shift to left or right...
comparisons: $<$, \leq , $=$, \neq , \geq , $>$: how to do?
- status flag register (ZF, SF, OF)
- Adder is the basic part for ALU
bit: $A+B$ (A, B is binary digit)
-> multiple addition: $AB+CD$



half adder implement

 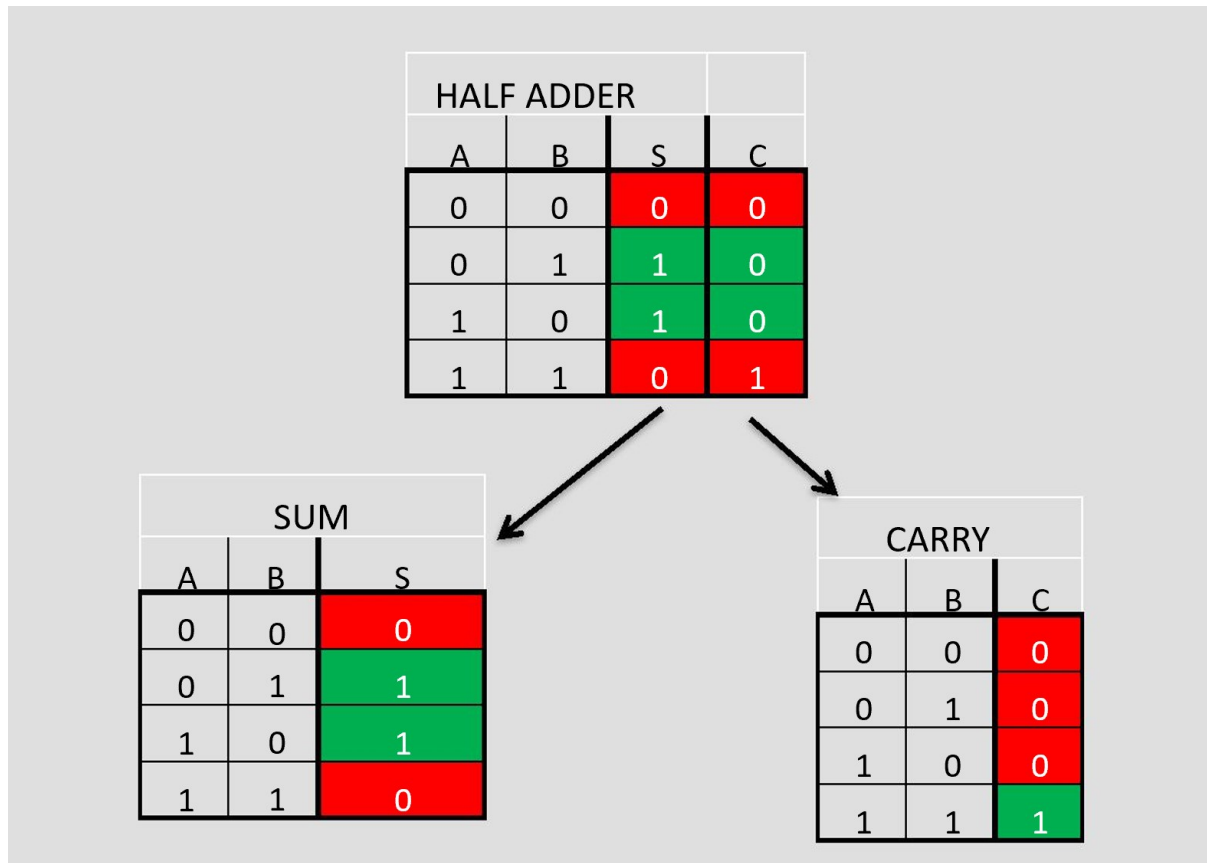

Use design rule to design full adder

A	B	C	S	D
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
1	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S=A'B'C+A'BC'+AB'C'+ABC$$

$$D=A'BC+AB'C+ABC'+ABC$$


it is useless to use kanoral for this one

Use two's half adder to design a full adder


$$S = A'B'C + A'BC' + AB'C' + ABC = C'(A'B + AB') + C(A'B' + AB) = C'(A \oplus B) + C(A \oplus B)' = C \oplus (A \oplus B)$$

[Use de Morgan law $A'B' + AB = (A'B + AB')'$ Convert them to basic gate form(XOR)]
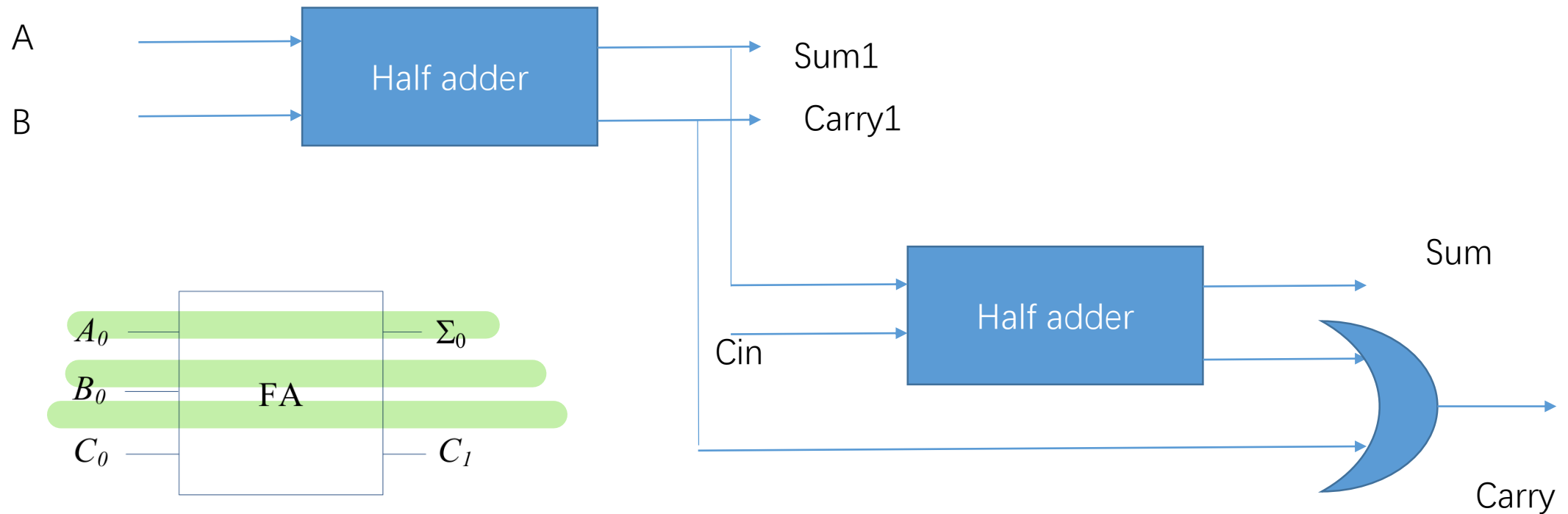
$$D = A'BC + AB'C + ABC' + ABC = AB + C(A'B + AB') = AB + C(A \oplus B)$$




Multi-stage full adder with ripple carry

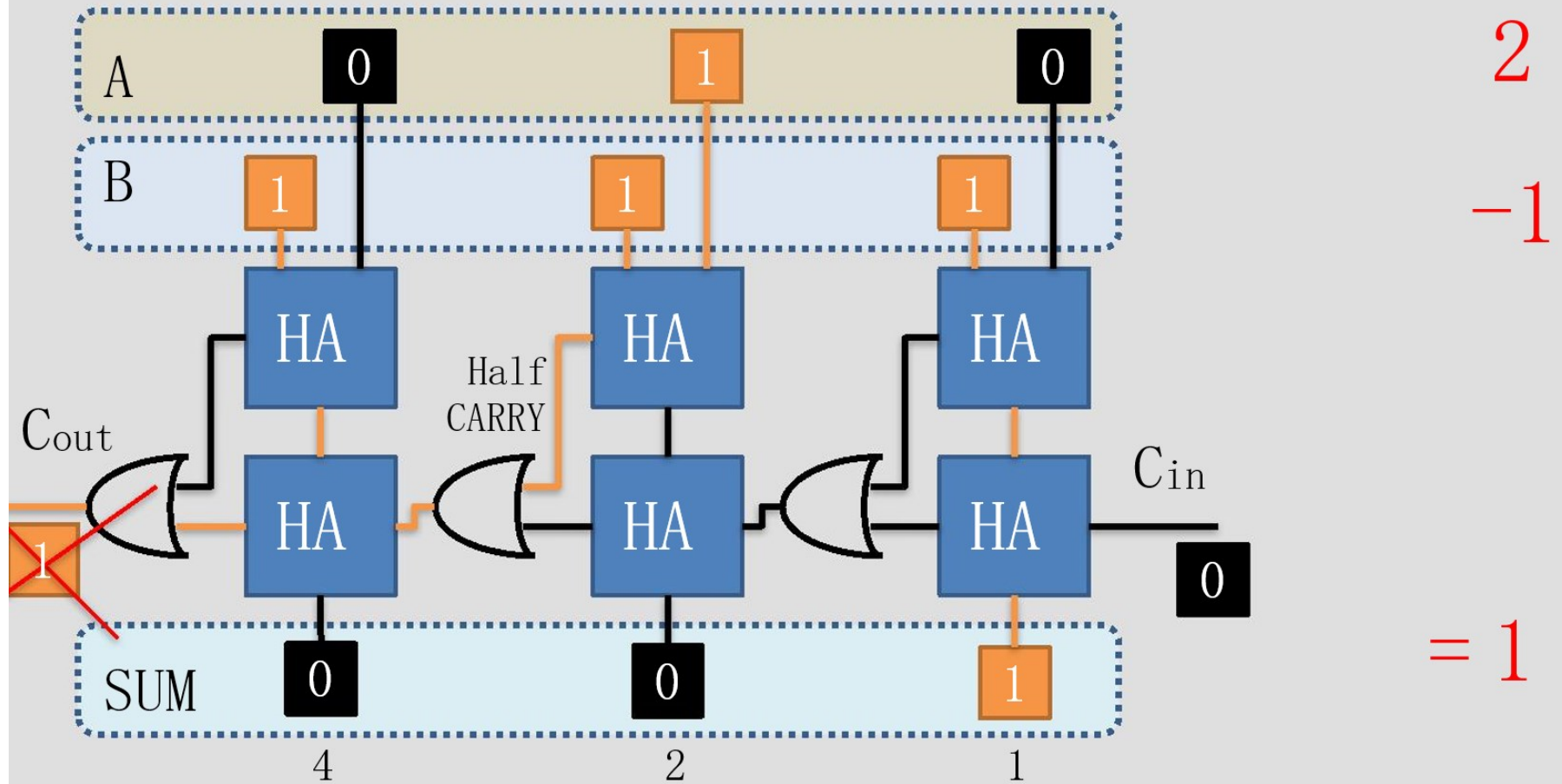

How to design subtractor

method 1

$$A - B = A + (-B) = A + (B' + 1)$$

 


method 2


A	B	D	B	
0	0	0	0	
1	0	1	0	
0	1	1	1	
1	1	0	0	

$$D = AB' + A'B$$

$$B = A'B$$

 

8 bits additions

 

4 bits subtraction

The status flags register

reflects an aspect of the outcome of the most recent ALU operation

Zero flag

Sign flag


Overflow flag

Judge the conditional branch according to flag register

-if($A > 0$)

-if($A == 0$)


-if($A < 0$)

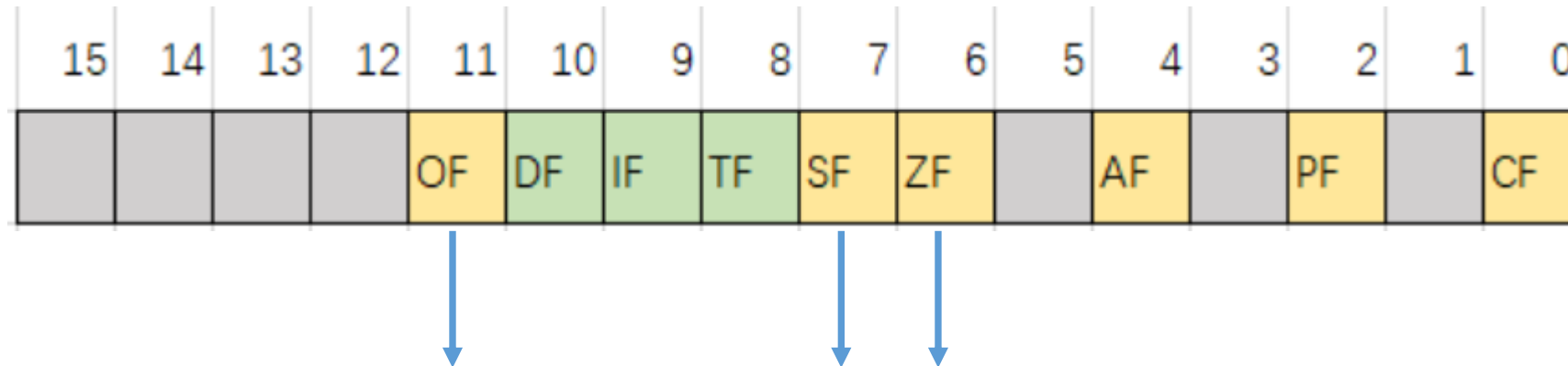

1 means the result status exist

Zero flags : and all bits

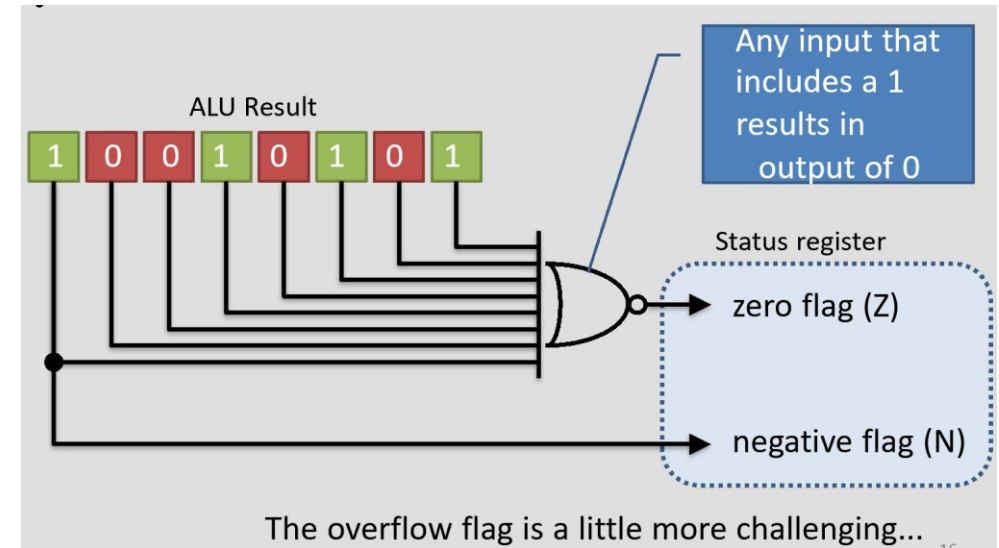Sign flags : Check the Sign bit of that number



Overflow flag: the result is too large to store

Carry flag: carry in or carry out

++ -> +
-- -> -

Data range

- For unsigned number N bits
data range: $0 \sim (2^N - 1)$
- For signed number
data range: $-(2^{N-1}) \sim (2^{N-1} - 1)$
- Example
- What is overflow
- 4 bits, $-8 \rightarrow 7$
- $4 + 4 = 1000(8) \rightarrow -8$, $-5 + (-5) = 0111 = 7$

How to design logic gates to detect overflow

1. S,A,B
2. Cin, Cout(most left-side bit)

A	B	C _{in}	S	C _{out}	OF
0	0	0	0	0	0
0	0	1	1	0	1
1	0	0	1	0	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	0	1	1
1	1	1	1	1	0

$$A'B'S + ABS'$$

$$CinCout' + Cin'Cout$$

1. $C_{in}=0, C_{out}=1, A=B=1$ overflow: two negative number addition
leftmost bits are both 1 (A and B are 1, we are adding two negative numbers and, getting a positively-signed result.
2. $C_{in}=1, C_{out}=0, A=B=0$; overflow: two positive number addition
leftmost bits are both 0 (A and B are 0), we are adding two positive numbers and getting a negatively-signed result
3. Other case: no overflow
 - a. $A=B=1, C_{in}=1, C_{out}=1$, two negative number addition, sum is negative
 $A=0, B=1; A=1, B=0$, or $S=0$; result can be positive and negative
(no overflow for different sign number addition: $-8 \rightarrow +7, 7-8=-1$)
 - b. $C_{in}=0, C_{out}=0$
where the leftmost bits are both 0, we are adding two positive and result is also positive. or where one leftmost bit are either 0 or 1
One positive plus one negative, result is negative

- 4+5
- 0100
- +0101
- 1001 (9) $C_{in}=1, C_{out}=0$
- -6-5
- 1010
- +1011 $C_{in}=0, C_{out}=1$
- 0001 (1)
- -3-4
- 1101
- 1100
- 1001 (-7)

-8	1000
-7	1001
-6	1010
-5	1011
-4	1100
-3	1101
-2	1110
-1	1111
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111

ALU other operation

➤ Comparisons

We can use 2's complement gives us subtraction
subtraction allows us to do comparisons: $<$, $>$, $=$
do “trial subtraction”, then check for +ve, -ve, or zero result)

➤ Multiplication and division?

Multiplication: shifting addition


Division: subtraction

➤ Logic operations can easily be built directly from logic gates



AND, OR, NOT, ...

Bit shifting

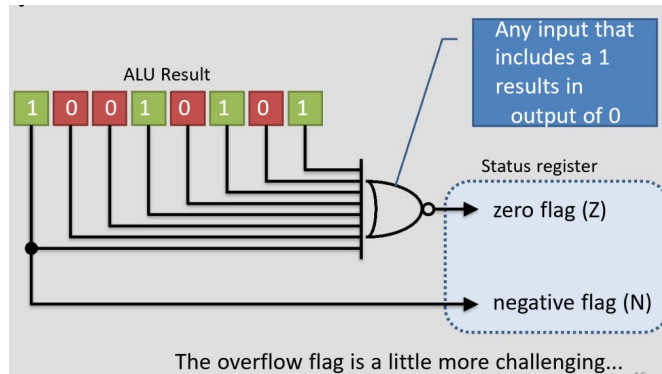As we've already seen, bit shifting enables simple multiplication/ division by powers of two, and can also speed up addition-based methods of multiplication, Movement of a bit pattern left or right is also widely used in control systems and pattern matching



Status Flag

 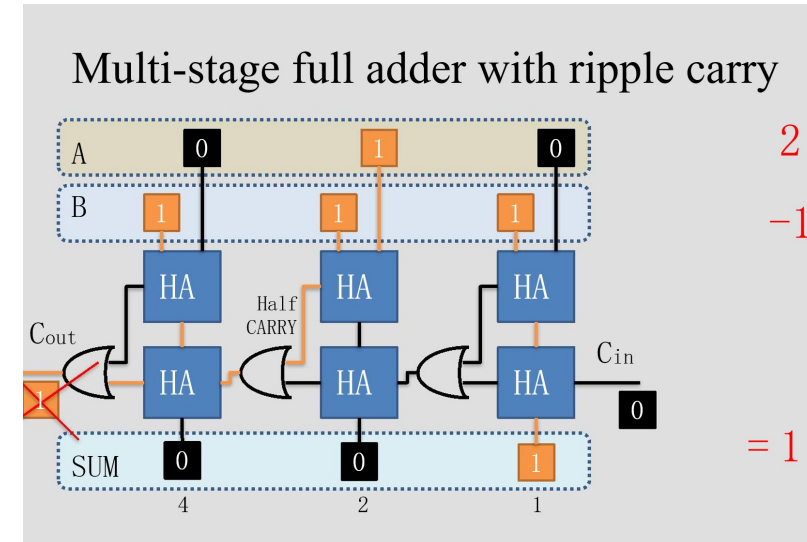

Shift

