

Topic 4: Building memory


Flip-flop 触发器

Register(寄存器) and Counter(计数器)

Combinational logic and sequential logic

- Combinatorial logic is that **its outputs are purely a function of its inputs** (ALU, voter, flags.....)
- Sequential logic is that its outputs are **a function of its inputs and of its current outputs(Register)**
 - This involves **feedback** of the outputs to the inputs
 - This feedback is the hook on which we hang memory(output remain)

S-R flip-flop

 

$R=S=0$, not allowed

Q_0	S	R	Q
0	1	1	0
1	1	1	1
0	0	1	1
1	0	1	1
0	1	0	0
1	1	0	0

$R=S=1$, Unchanged

$S=0, R=1; Q=1$ set

$S=1, R=0; Q=0$ reset

RS flip-flop

Feedback is introduced, Output Q_{n+1} is related to original Q_n

R,S can set or reset output


R,S=1,the output remain (keep unchanged), It means this bit is reserved

Basic logic gate for sequential circuit(state equation): $Q_{n+1} = S' + QR$:


Limitations of the S-R flip-flop

- There are two problems in using an S-R flip-flop to implement a bit in a register
 1. It has distinct SET and RESET inputs
 - We'd ideally like just a **single input** that “sets” the state if it's 1 and “resets” the state if it's 0
 2. We have no way of telling the flip-flop exactly **when** it should store input data
 - We'd like a “**latch**” signal for this to work in a practical system under the supervision of a **control unit**

 
Add a latch as control to two gates , D is input data



D-latch

 

Q_0	D	L	Q	
0	0	0	0	
1	0	0	1	
0	0	1	0	} "latch" a 0
1	0	1	1	
0	1	0	0	
1	1	0	1	
0	1	1	1	} "latch" a 1
1	1	1	1	


 


D latch symbol

Difference from RS flip flop

- One input $L = 1, Q_{(n+1)} = D$
- One control (Latch) $L = 0, Q = Q_0$

D flip flop

  


In what case, $Q=D$? Benefit?

上升沿触发，脉冲触发，在瞬间触发，降低干扰

what's meaning of D , Q , CP , Q'
 D : input data
 Q : output
 Q' : the reverse of output
 CP : clock pulse

Waveform 波形
Draw Q1, Q


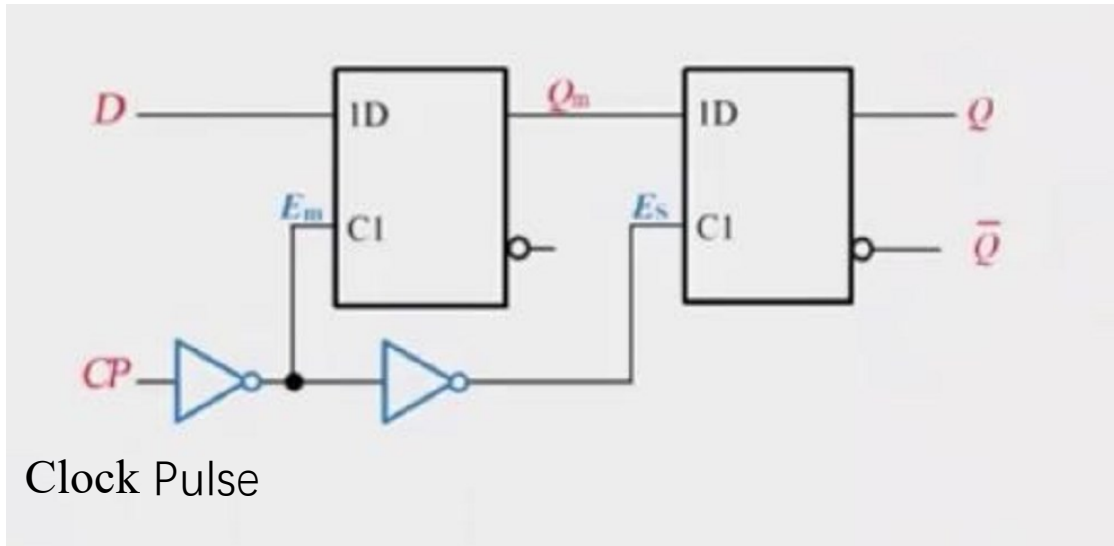


D0 is effective input
 D1, D2, D3 are interference
 D4 is effective input
 Only D1 and D4 are reserved

CP control to store


Compare Q1, Q,
 Q1: interference
 Q: No interference
 In CP edge, Q=D

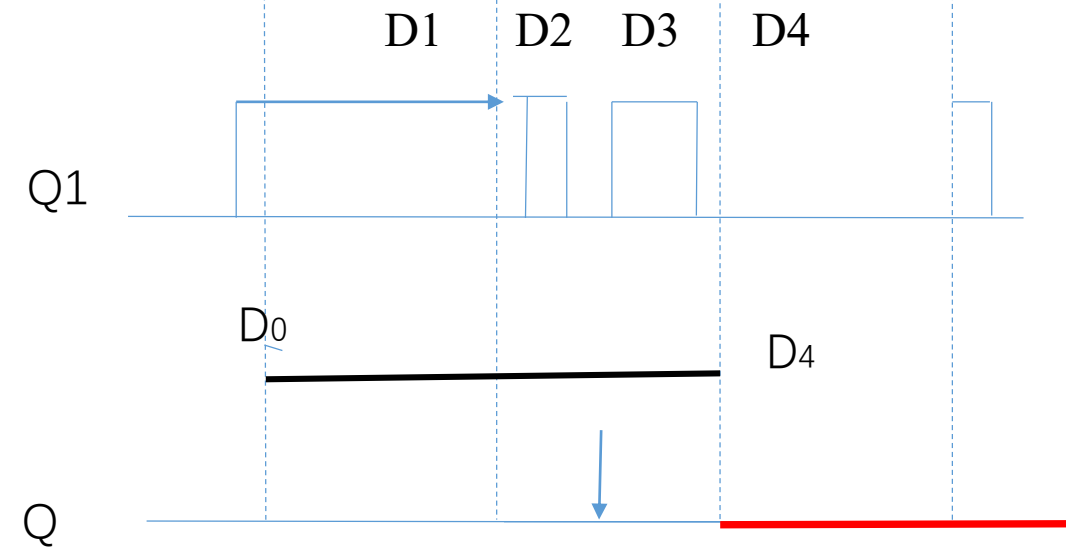 CP=0, 外部信号进入Q1, Q不变
 CP=1, Q1进入Q输出, 外部信号不进入, D1,D2,D3抑制



Assume: interference

Where is CP from?

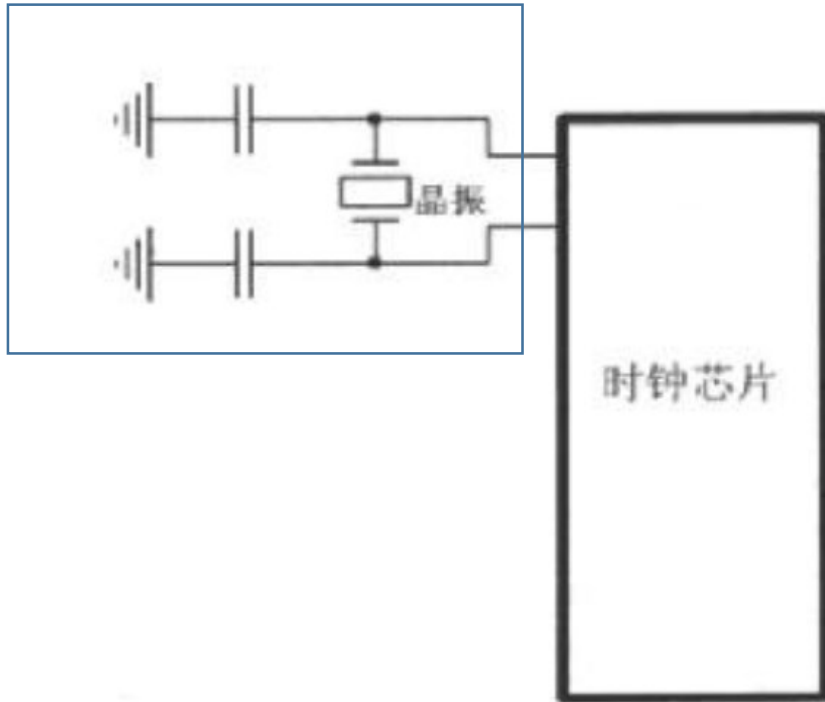


CP is control signal, which input to control unit of each computer components

Clock pulse circuit


How to build register?

A register using multiple flip-flops

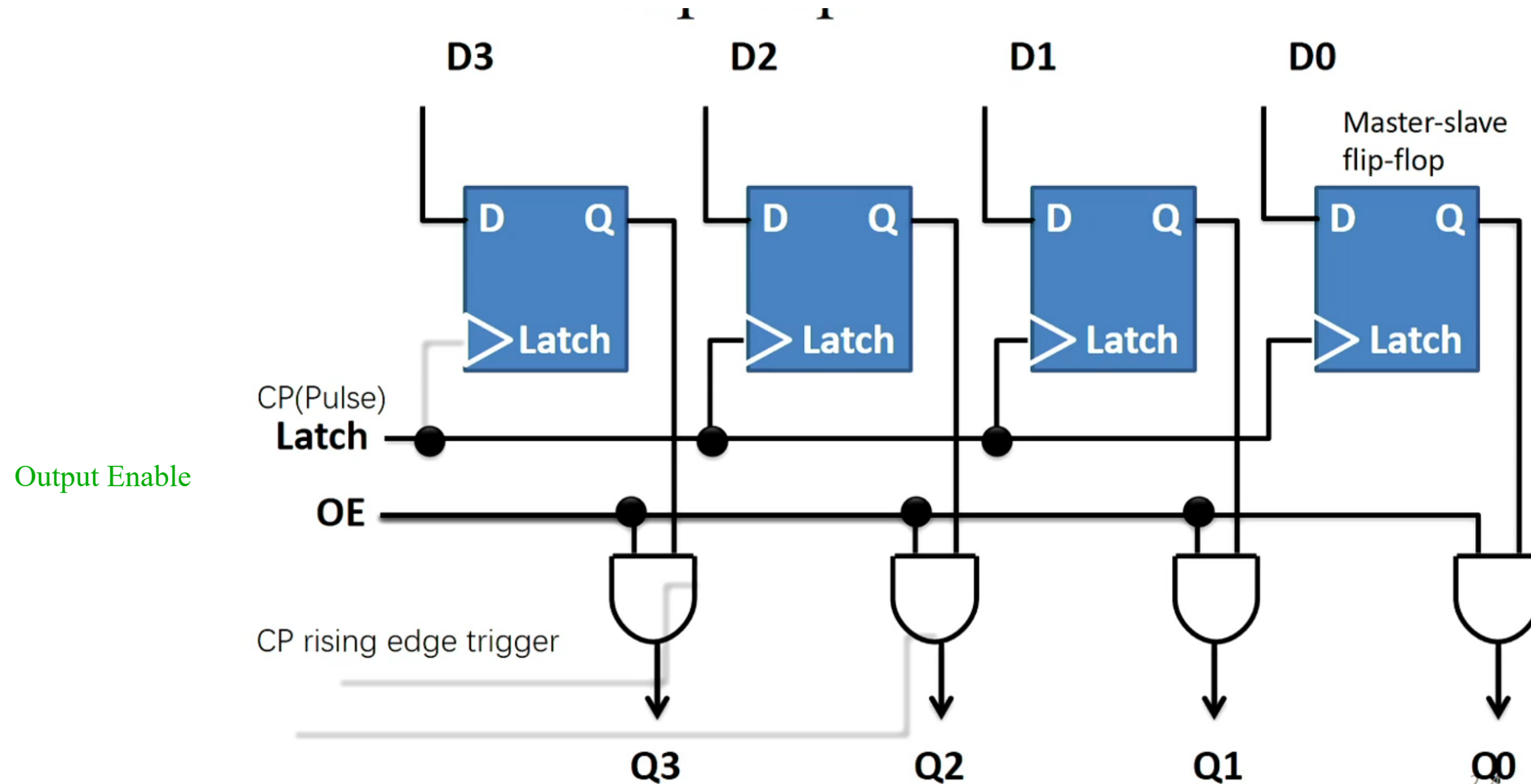

Draw the sequential diagram Analyze the logic gate function

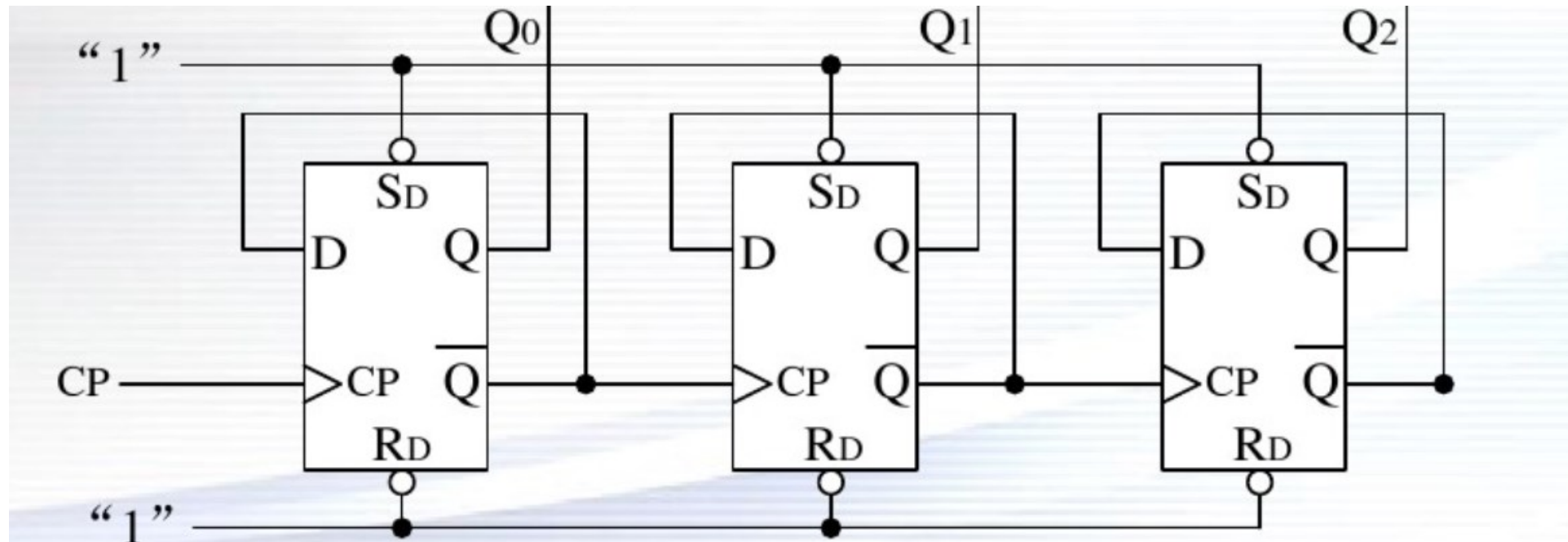
(S is set control, R is reset control, assume $Q_0=0$, $Q'_0=1$)
(low level is effective)




Write logic status equation

Draw sequential waveform




 


Base 4

 


Countdown counter

 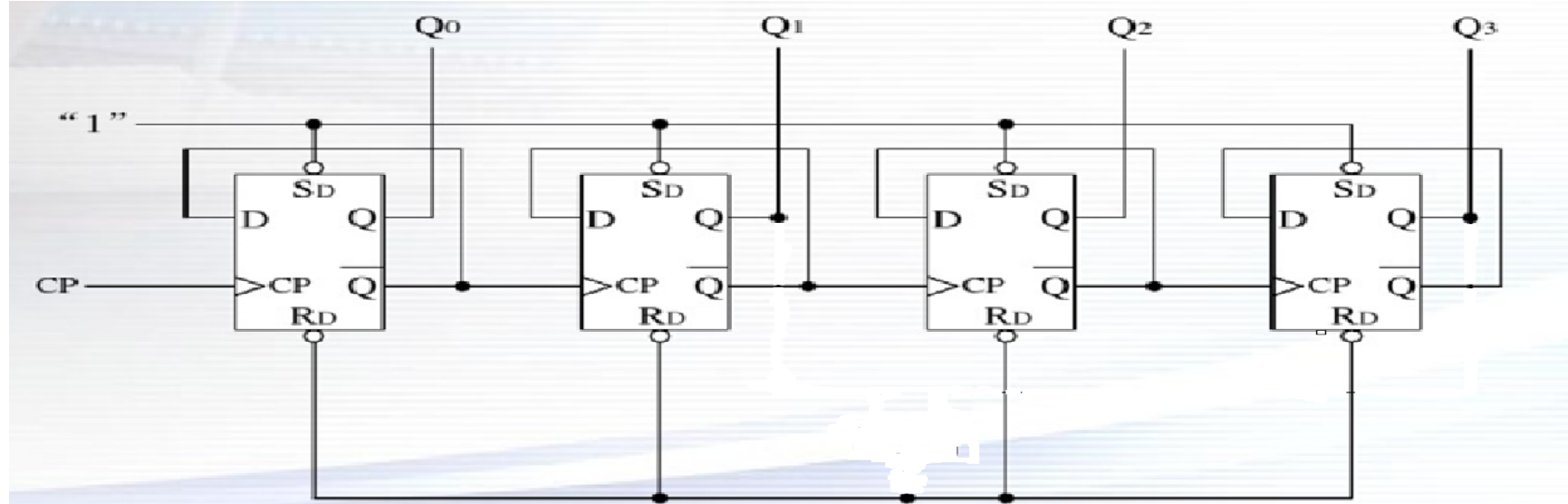(S is set control, R is reset control, assume $Q_0=0$)



Counter (Timer)
Frequency divider

Shift right register

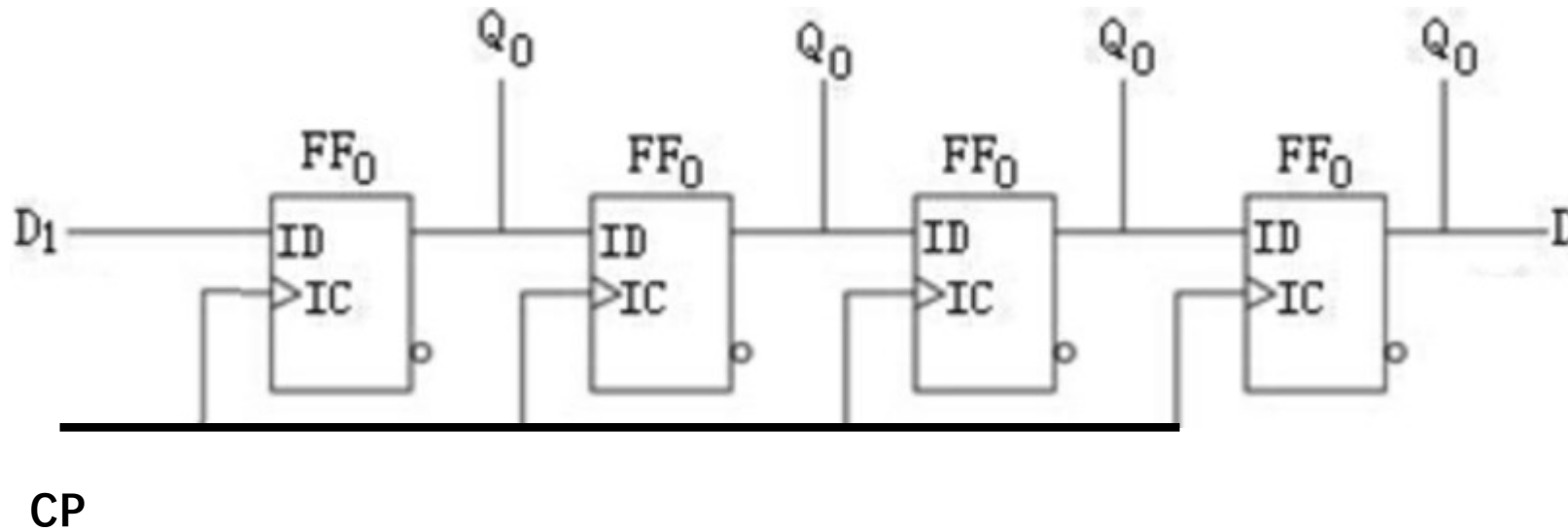


Serial input D_1 and parallel out

shifting right

synchronous trigger

Shift right register

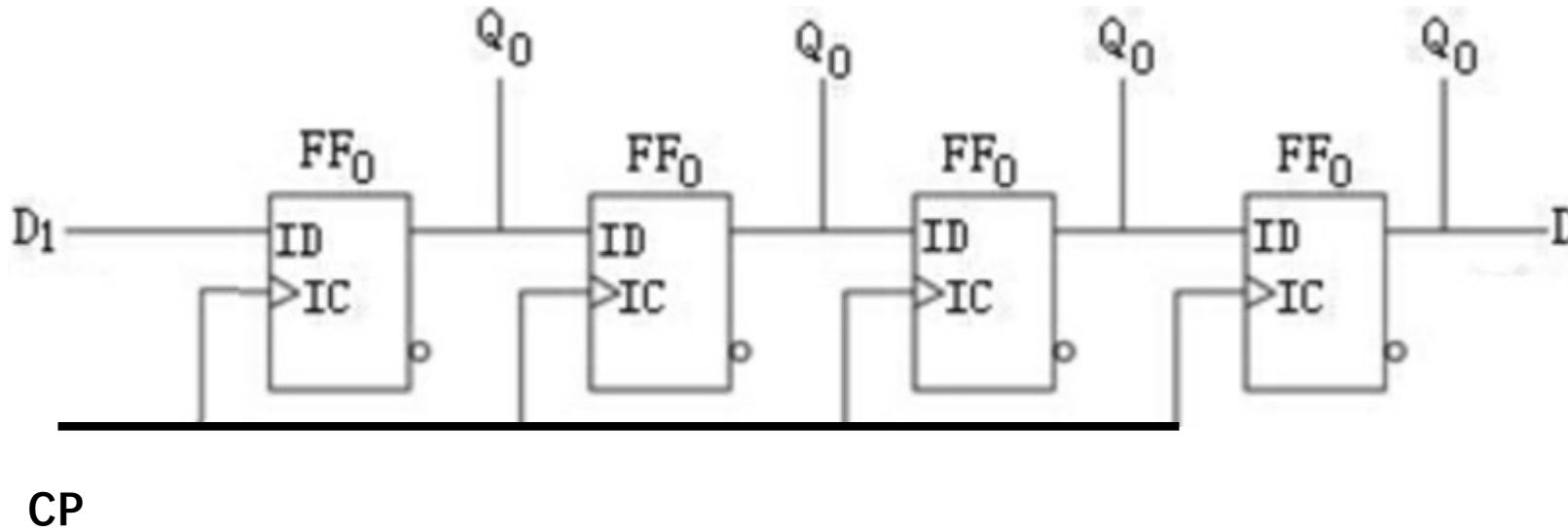


Serial input D_1 and parallel out

shifting right

synchronous trigger

Loop shift register

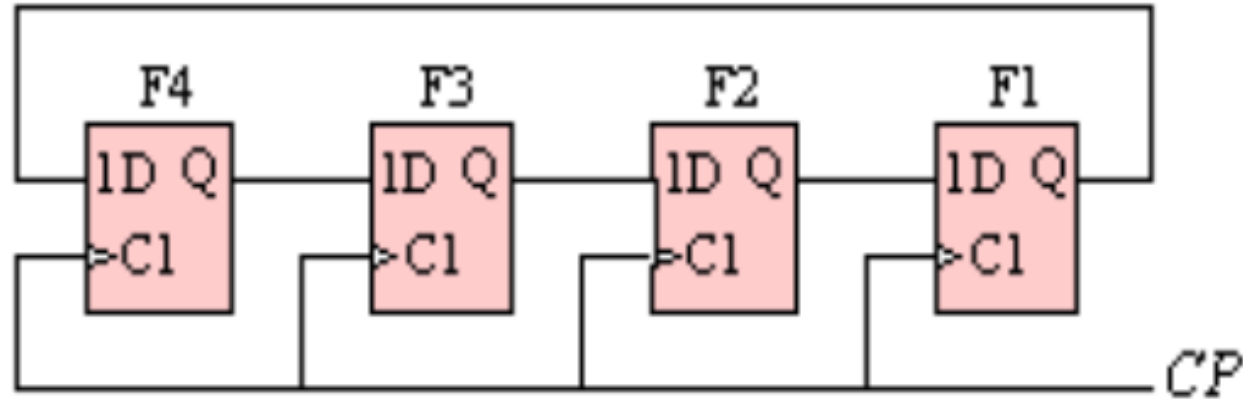

Loop

Initial state: F4F3F2F1:1000

	F4	F3	F2	F1
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	0	0	0


Buses: connecting the blocks

- Buses are the “glue” of the computer architecture
 - They connect the elements of the von Neumann architecture: the ALU, the control unit, memory chips, and I/O devices
 - They are essentially bundles of **wires**, one for each bit
- There are three types of bus
 - *An address bus runs between the control unit and main memory*
 - Used to tell main memory to access a specific address (whether for reading or writing)
 - The “width” of the address bus corresponds to the amount of addressable memory
 - Examples: 16 bits \rightarrow 65536 bytes (2^{16}); 32 bits \rightarrow 4 GB (2^{32})
 - *Data buses carry data around the computer*
 - An “n-bit” processor will have a data bus n bits wide (e.g. $n=8$ or 32 or 64)
 - This means we can read/ write n bits from/ to memory in one go
 - Some processors have distinct internal and external data buses
 - External bus may be narrower to reduce the number of external connections/ pins, and thus cost
 - *Control bus*

Data buses: connecting to registers

Explanation

- Bus wires are *shared*

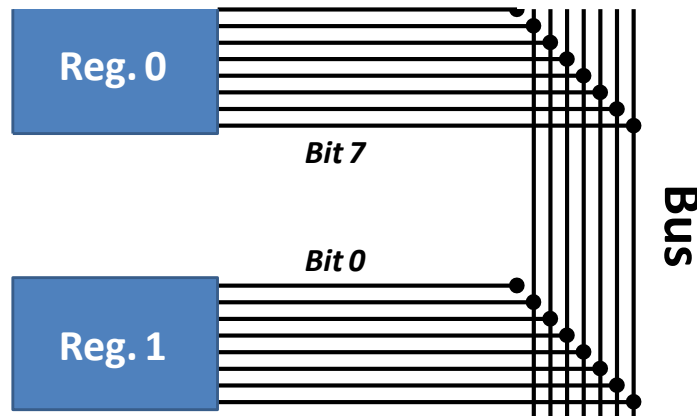

... so we must ensure that there is only one active output at a given time?

A job for **output enable**...

Summary

- We know the difference between **combinatorial and sequential logic**
- We know how logic components can be used to **build one bit of static storage** (static memory) **flip flop**
we know how these bits can then be combined into multi-bit
Registers and counter
- We understand how the elements of the computer architecture can be glued together using **buses**

Exercise

1: Draw out the **D flip-flop symbol**, explain the meaning of CP, D, Sd, Rd, Q, Enable.

2: Draw base-6 counter logic circuit

Draw the waveform of base_6 counter

3. Design any number system counter(任意进制, 如54进制, 前50个10进制, 后4个位5进制)

Exercise after class

- Design 60 base counter
- Design a timer(counter based on subtraction)