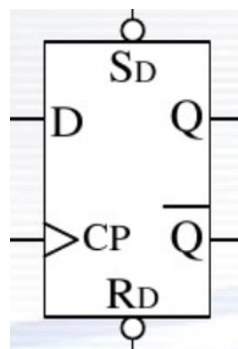


Practice 4 Flip flop and counter

1. D flip flop test

74LS74 is ascending edge trigger D flip-flop (from 1 to zero). 74LS74 has two internal D flip-flops. The truth table of 74LS74 can be found in your system. Your task is to test and fill in the truth table.

- 1、 Test S_d (set), R_d (reset) function
- 2、 CP is clock pulse (press button switch on and down)
- 3、 Q^n , Q^{n+1} stand for previous state and current state
- 4、 D is input, Test D flip-flop function, that is to let $D=0$, $D=1$, use single pulse or to observe the output
(S_d , R_d set or reset, then $S_d=R_d=1$)



CP



$Q=D$


Q is unchanged


at CP rising edge

at others


\bar{S}_d \bar{R}_d	CP	D	Q^n	Q^{n+1}
0 1	X	X	1	
			1	
1 0	X	X	0	
			0	
1 1		0	0	
			1	
1 1		1	0	
			1	
1 1	0 (1)	X	0	
			1	

CP

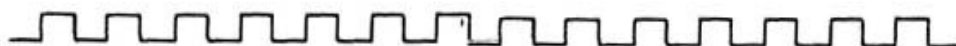

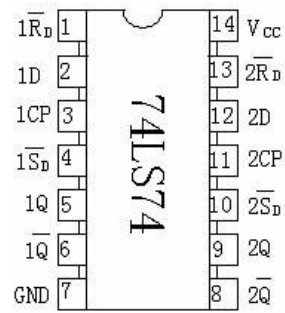

2. Use D flip-flop build counter

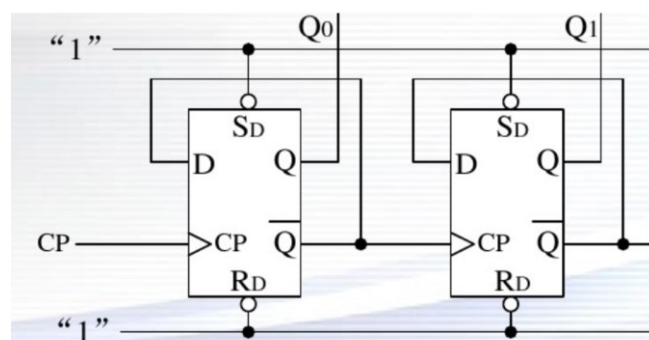

Base 4 counter

3. Use logic analyzer to observe the base4 counter waveform